
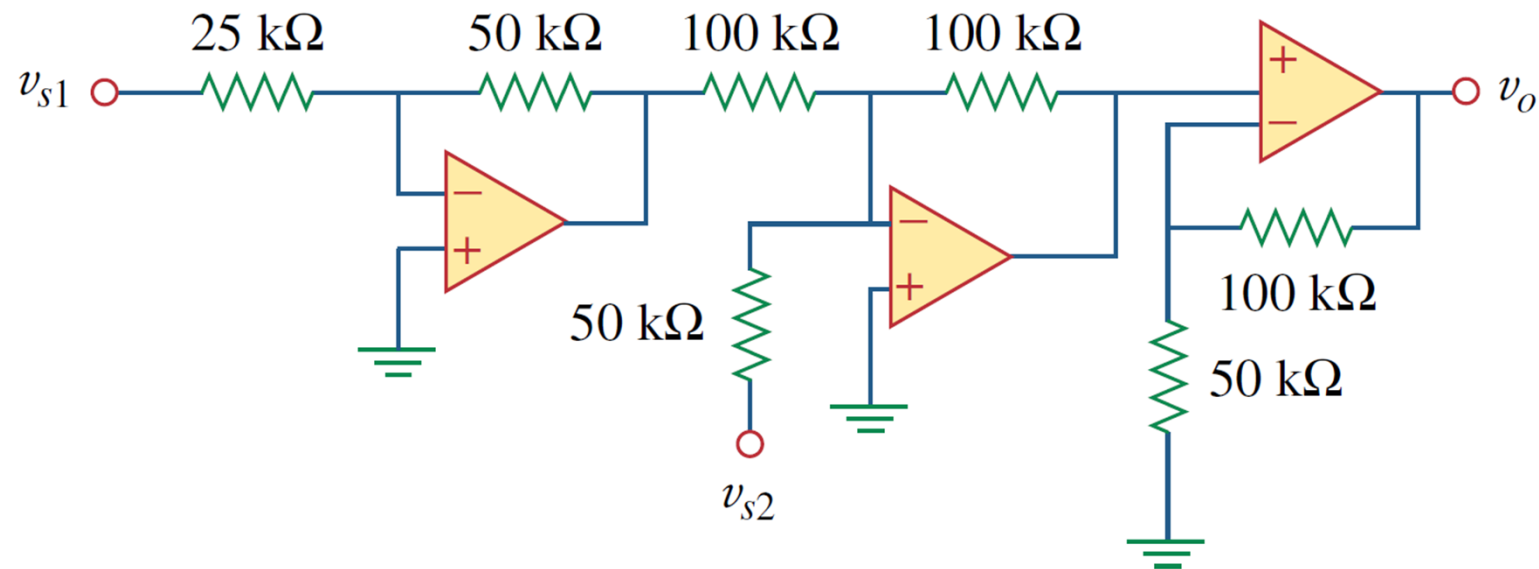


Assignment

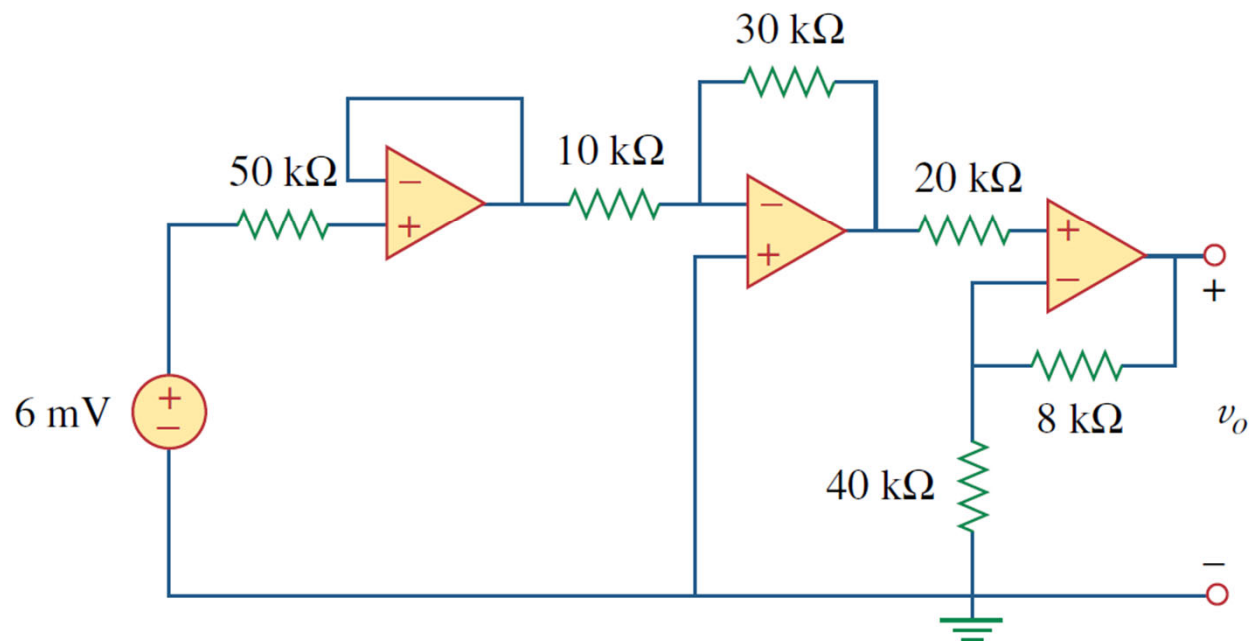
5.57 Find v_o in the op amp circuit of Fig. 5.84.




5.65 Find v_o in the op amp circuit of Fig. 5.92.



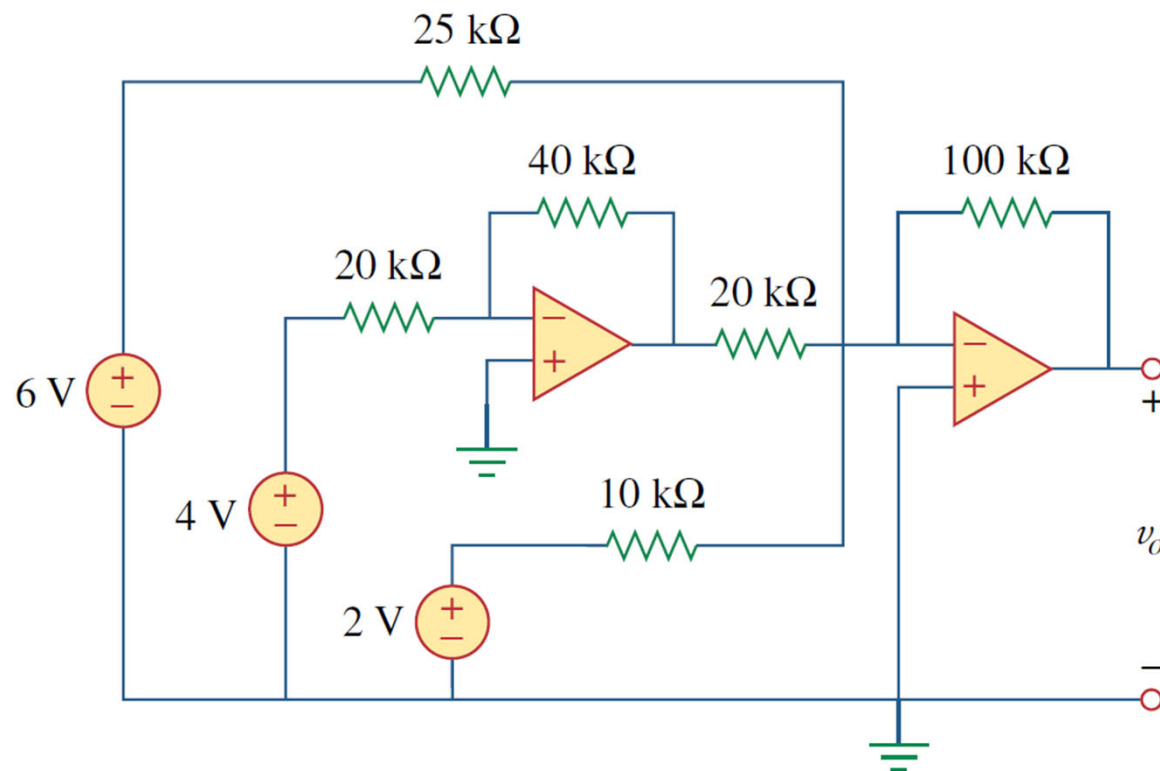
5.66 For the circuit in Fig. 5.93, find v_o .



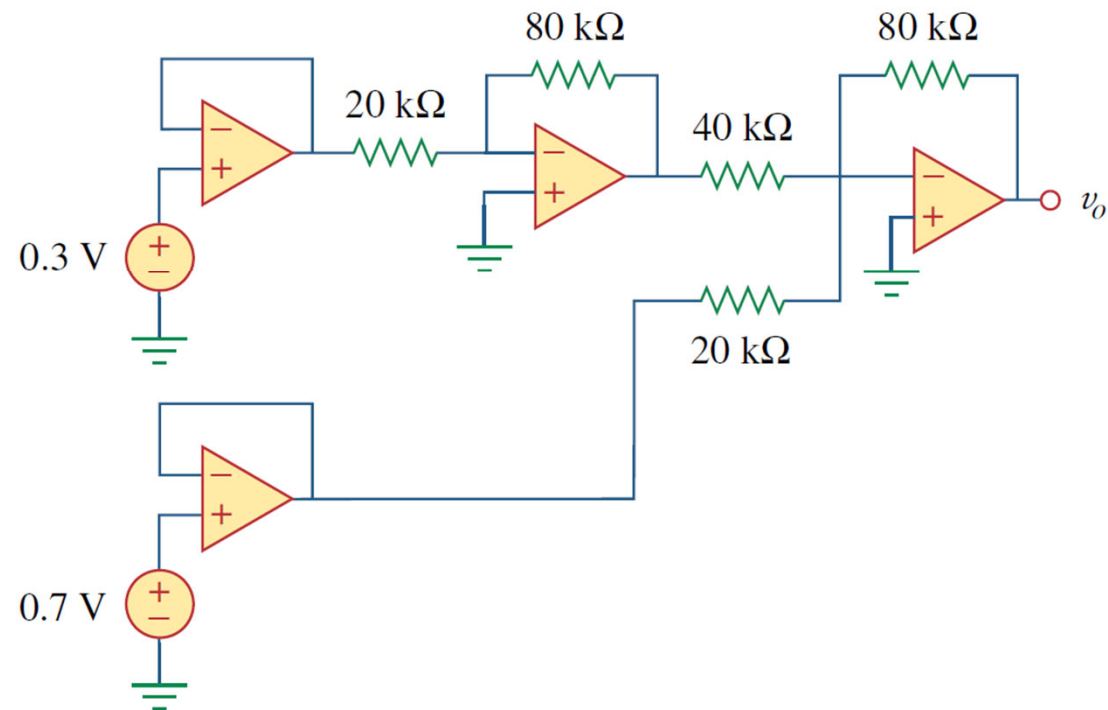
5.67 Obtain the output v_o in the circuit of Fig. 5.94.



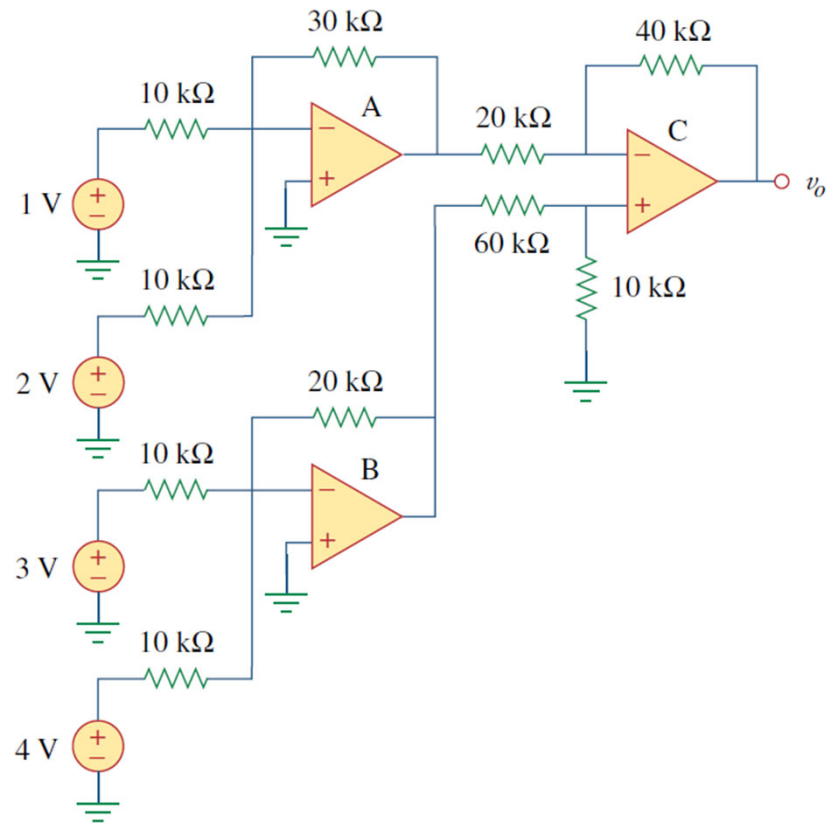5.70 Determine v_o in the op amp circuit of Fig. 5.96.



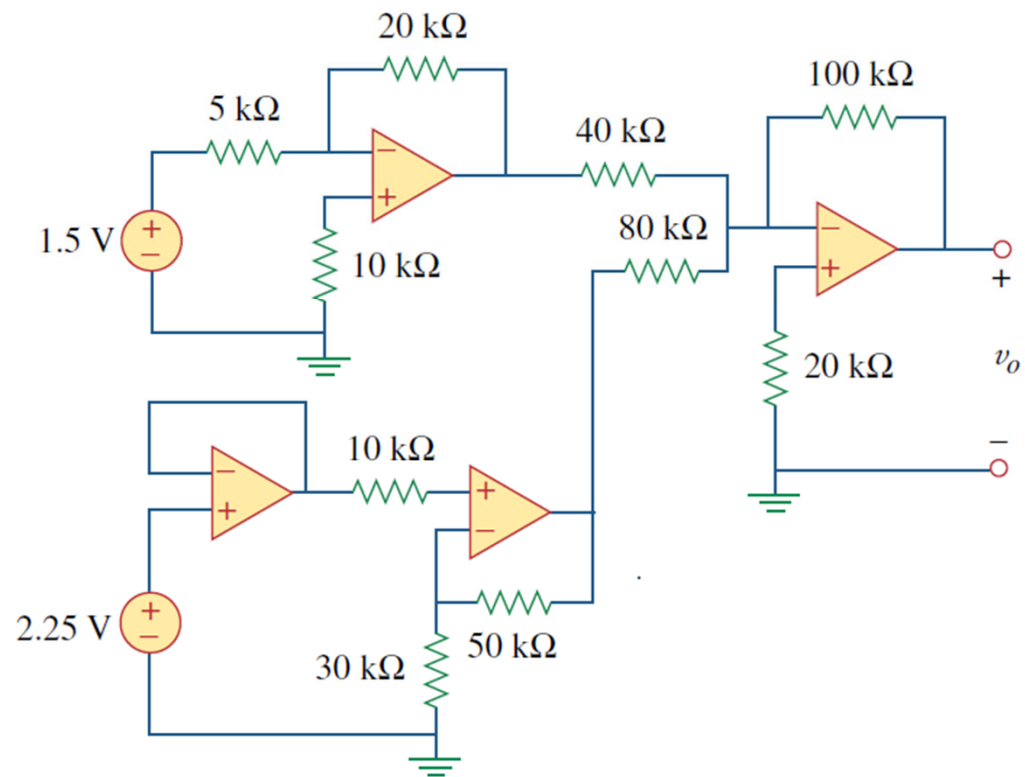5.71 Determine v_o in the op amp circuit of Fig. 5.97.



5.74 Find i_o in the op amp circuit of Fig. 5.100.

