

1.2 Determine the current flowing through an element if the charge flow is given by

(a) $q(t) = (3t + 8) \text{ mC}$

(b) $q(t) = (8t^2 + 4t - 2) \text{ C}$


(c) $q(t) = (3e^{-t} - 5e^{-2t}) \text{ nC}$

(d) $q(t) = 10 \sin 120\pi t \text{ pC}$

(e) $q(t) = 20e^{-4t} \cos 50t \mu\text{C}$


Assignment

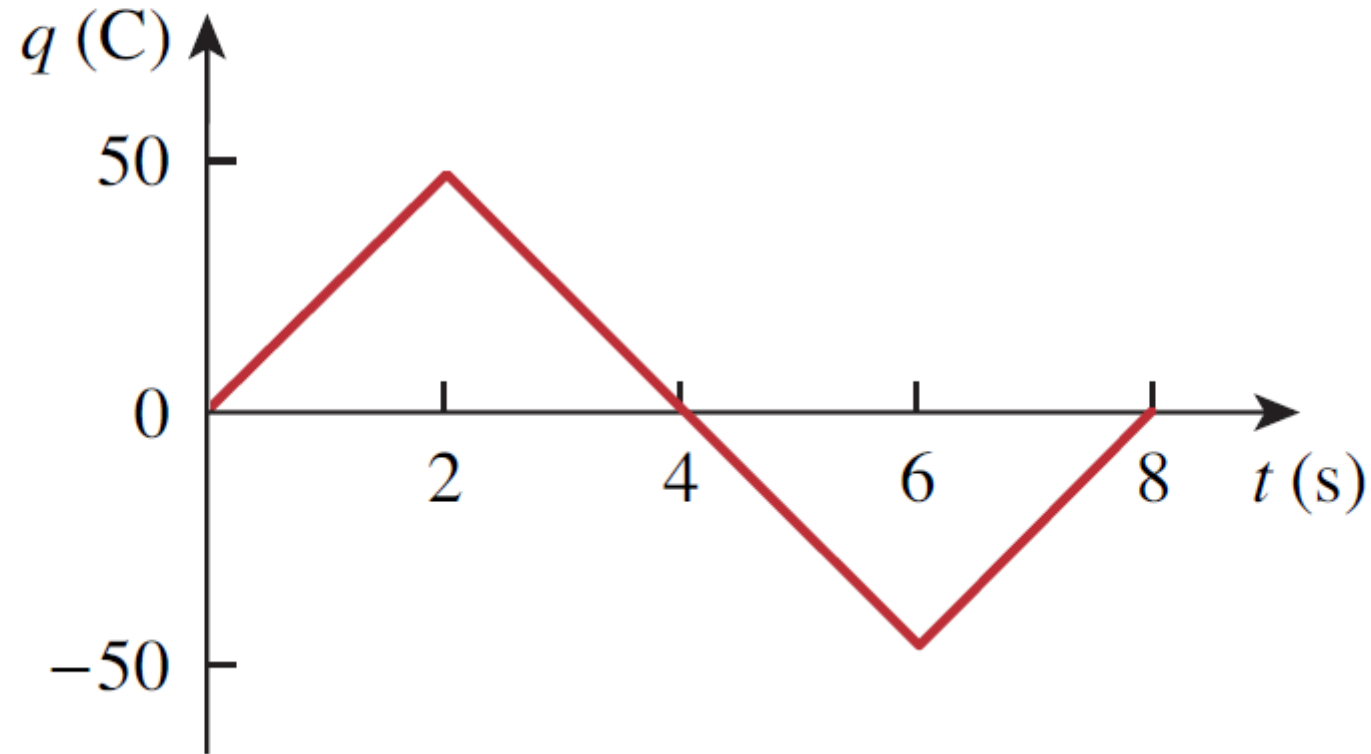1.7 The charge flowing in a wire is plotted in Fig. 1.24. Sketch the corresponding current.



Assignment

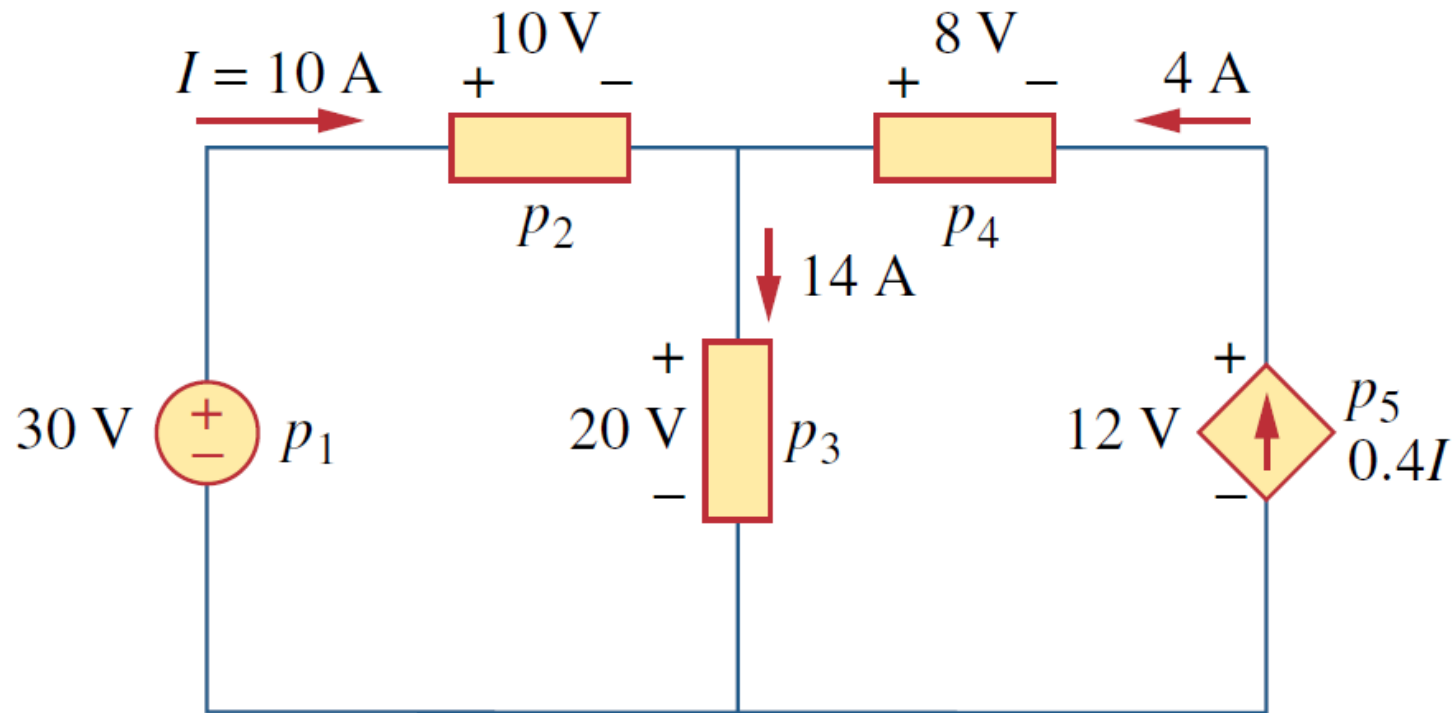1.18 Find the power absorbed by each of the elements in Fig. 1.29.



Assignment

1.20 Find V_o and the power absorbed by each element in the circuit of Fig. 1.31.

