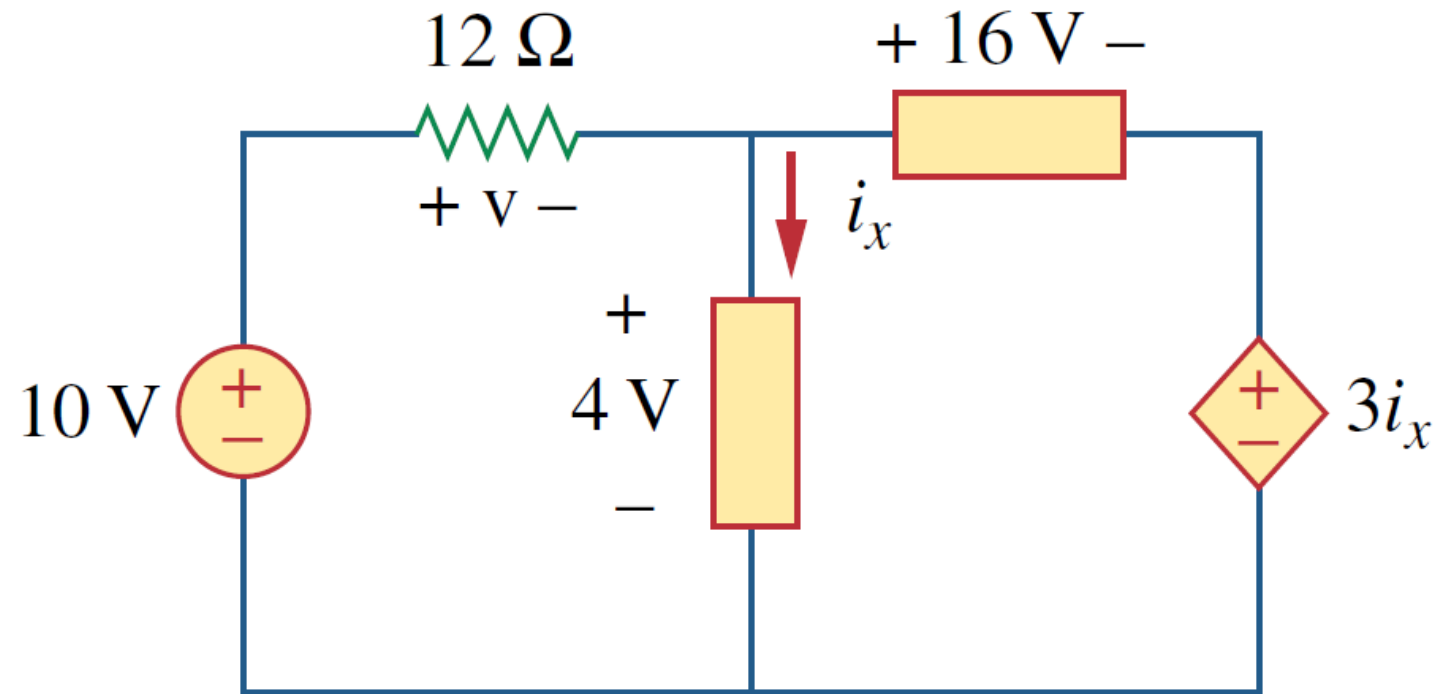



# Assignment 2

**2.15** Calculate  $v$  and  $i_x$  in the circuit of Fig. 2.79.



**Figure 2.79**  
For Prob. 2.15.


**2.22** Find  $V_o$  in the circuit in Fig. 2.86 and the power absorbed by the dependent source.

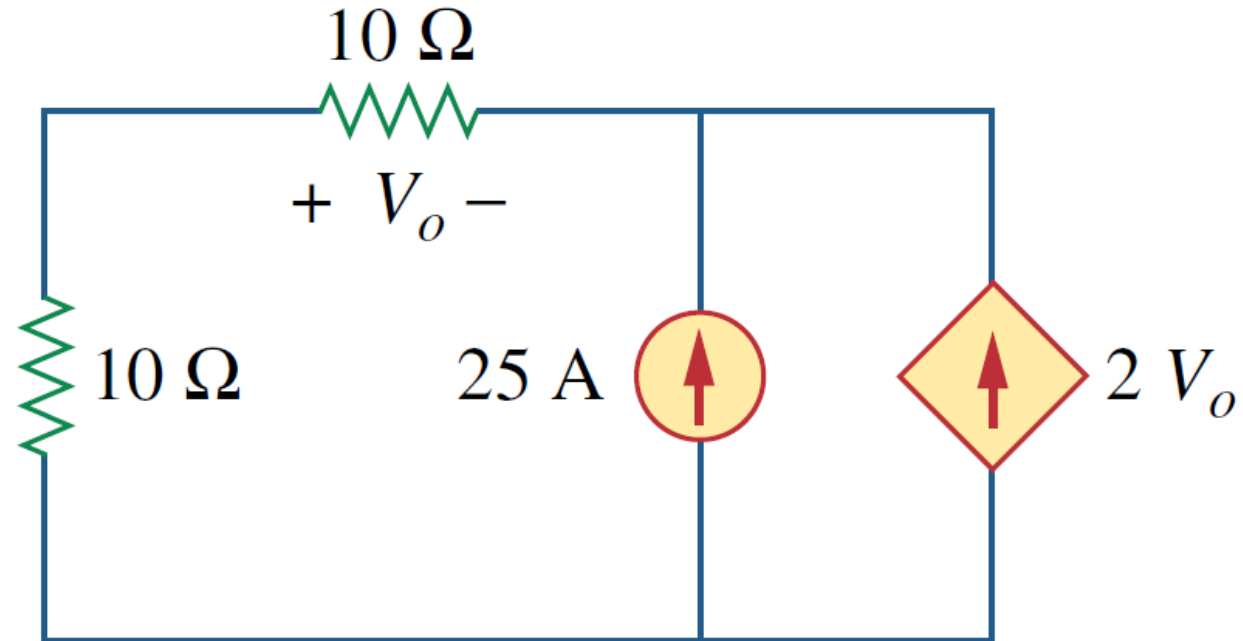

**Figure 2.86**


For Prob. 2.22.

**2.25** For the network in Fig. 2.89, find the current, voltage, and power associated with the 20-k $\Omega$  resistor.

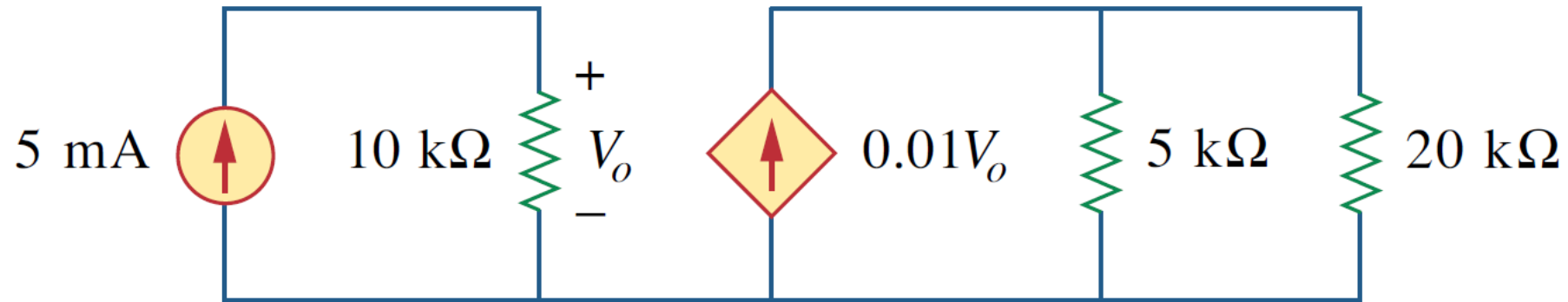

**Figure 2.89**  
For Prob. 2.25.


**2.36** Find  $i$  and  $V_o$  in the circuit of Fig. 2.100.

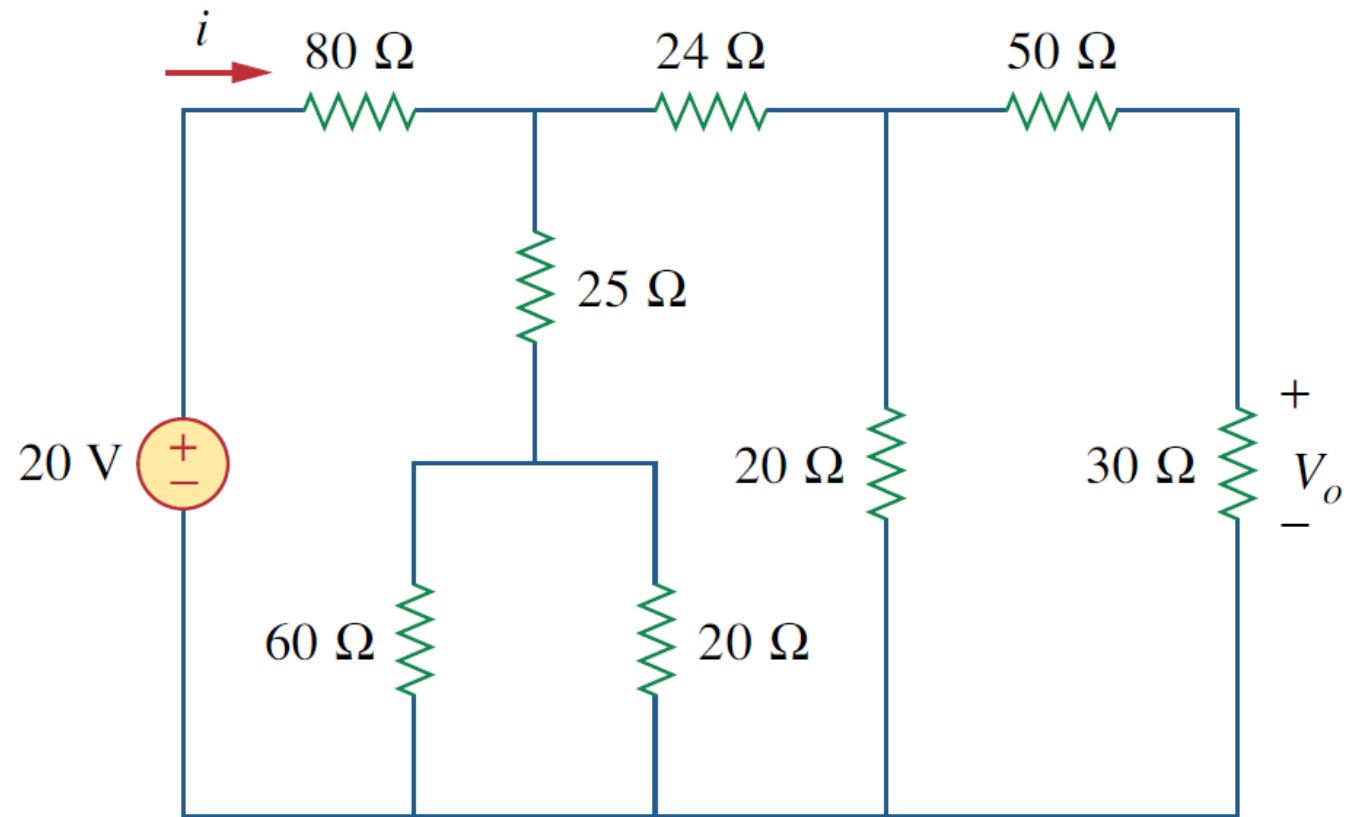

**Figure 2.100**

For Prob. 2.36.


**2.41** If  $R_{eq} = 50\ \Omega$  in the circuit of Fig. 2.105, find  $R$ .

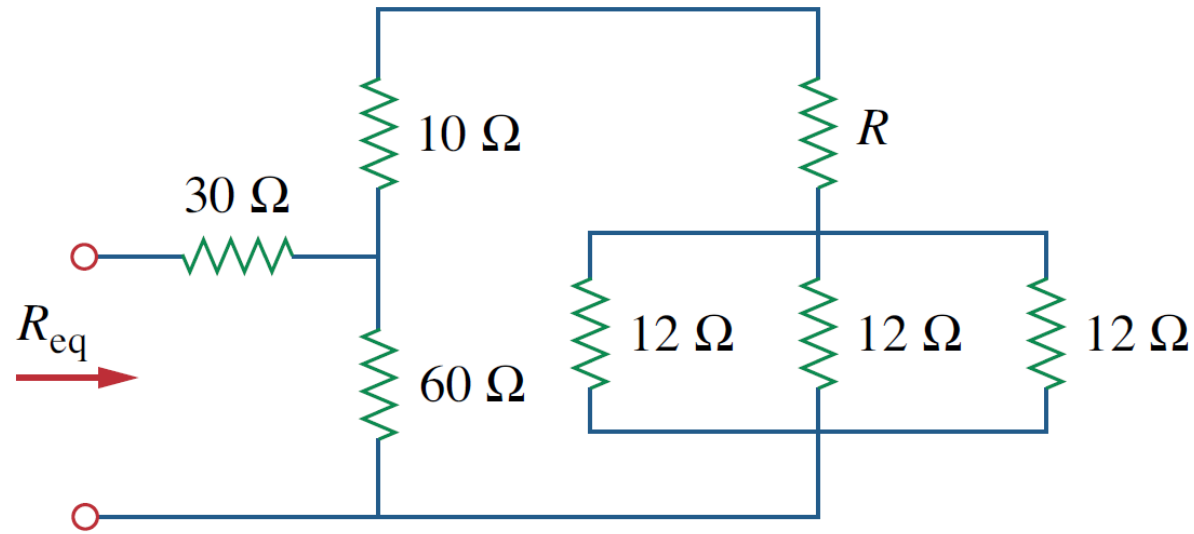


**Figure 2.105**

For Prob. 2.41.

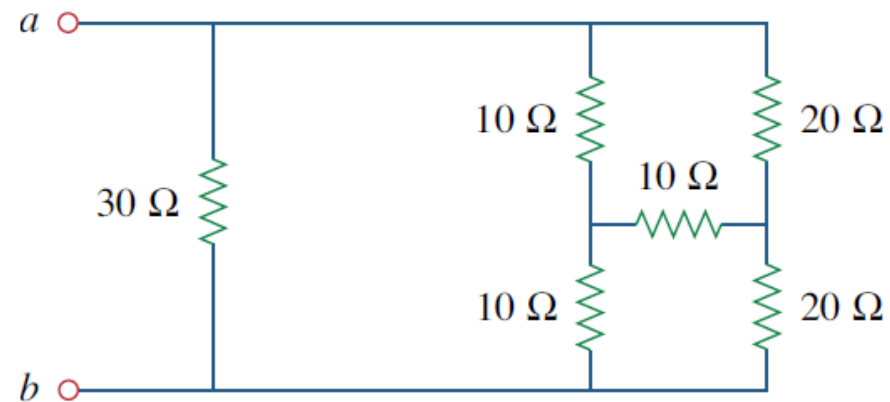**2.51** Obtain the equivalent resistance at the terminals  $a$ - $b$  for each of the circuits in Fig. 2.115.



(a)

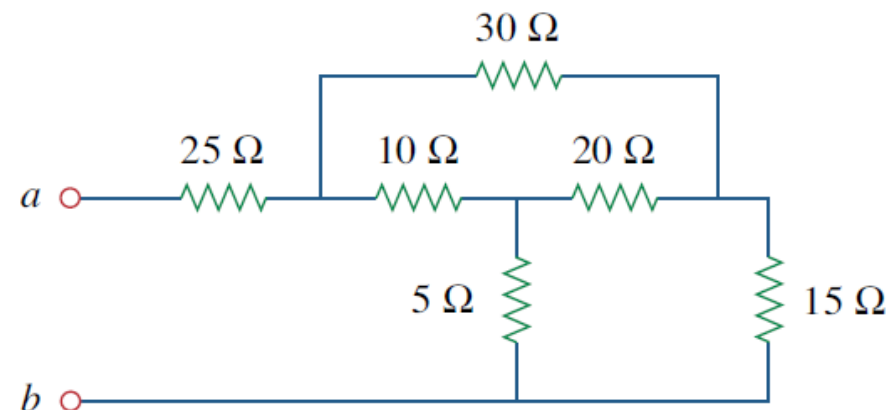

(b)

**Figure 2.115**  
For Prob. 2.51.